DAB Converter Design Using Scaling Laws

Nicola Rosano

September 22, 2022 10 am California time 7 pm Italian time

Why Another Topology?



What is the meaning of DAB?

- « DAB » means <u>D</u>ual <u>A</u>ctive <u>B</u>ridge and identifies an isolated power stage topology in which you can identify two Full Bridges.
- Both bridges are intended to be Active and each power switch is turned ON and OFF according the designer's needs. The primary bridge acts as inverter, the secondary one acts as rectifier. Vice versa if we reverse the power flow.



All switches have the same switching frequency
 All switches modulation angles are Q1 referenced



3. The lag between the two high side FETs is D1 × π (radians), and since D1 can be maximum 1, the maximum shift is π radians or 180°. **D1** thus corresponds to what we may refer alternately to as "**Angle 1**", or "**intra-bridge angle**"



4. Similarly, the lag between Q1 and Q5 is D2 × π (radians). **D2** corresponds to what we may refer alternately to as "**Angle 2**", or "**inter-bridge angle**".



5. Each bottom switch is driven complementarily to its top switch to avoid Shoot-Through Current.



Timing: Step 1/4 Angle1 = 100°, Angle2 = 60°, gain = 1 (8 intervals worst case)

- Removing C_dc_block and Lmag: not relevant for the analysis
- Remove the transformer: it's just a scaling factor
- Q1,Q6,Q8,Q4 ON \rightarrow Circulating current on the secondary
- No power delivered to the load





Timing: Step 2/4 Angle1 = 100°, Angle2 = 60°, gain = 1 (8 intervals worst case)

- Angle2 < Angle 1 \rightarrow Q5 (Angle 2) closes first than Q3 (Angle 1)
- Q6 moves complementary to Q5
- Power delivered to the load



$$V_{Llk} = V_p - V_s = V_a - V_b - (V_c - V_d)$$



Timing: Step 3/4 Angle1 = 100°, Angle2 = 60°, gain = 1 (8 intervals worst case)

- Q3 (Angle 1) closes after than Q5 (Angle 2)
- Q4 moves complementary to Q3
- Circulating current on the primary
- Power delivered to the load





Timing: Step 4/4 Angle1 = 100°, Angle2 = 60°, gain = 1 (8 intervals worst case)

- Q7 (Angle 1+Angle 2) closes after than Q3 (Angle 1)
- Q8 moves complementary to Q7
- Fully "circulating" (zero) current
- No power delivered to the load



- Complementary 4 cycles start later!
- The leakage current becomes negative
- worst case: 8 segments Leakage Voltage



A unique DAB design approach

- Study a kernel with random values
- Apply Maniktala's scaling laws and use Rosano's graphical curves

Targets:

- Soft Switching
- Lower RMS currents possible
- Optimal Power shape

Design:

- Leakage inductance
- Turn ratio
- Output capacitance
- DC blocking capacitance (optional)
- Angle 1 and Angle 2 selection

Definitions:

- *V_{or}* is the ouput voltage reflected on the transformer primary side
- V_{in} is the input bus voltage
- $Gain = \frac{V_{or}}{V_{in}}$, ratio between Llk amplitude voltage extrema
- Do not confuse the «gain» with the transformer turn ratio $N = \frac{N_p}{N_s} = \frac{V_{or}}{V_{sec}} = \frac{V_{in} \cdot gain}{V_{out}}$

The Scaling laws: « three is a magic number! »

- To double the power at a certain frequency (keeping all else unchanged such as the phase angles), we need to halve the inductance and double the capacitance.
- To double the frequency, keeping the same power, once again we just need to halve the inductance and halve the capacitance. Recalling the buck converter equations.

$$L = \frac{V_{out} \cdot (1-D)}{r \cdot f_{sw} \cdot I_{out}} \qquad C = \frac{I_{out} \cdot r}{8 \cdot f_{sw} \cdot \Delta V} \qquad r = \frac{2 \cdot I_{ac}}{I_{dc}}$$

• Added guest to the party: If we double the input voltage, we will quadruple the power. Proof below:

lf:

$$P_{out} \cong P_{in}$$
$$V_{out} = TF_{dc} \cdot V_{in}$$

then:

$$\blacktriangleright P_{out} = \frac{V_{out}^2}{R_{load}} = \frac{(TF_{dc} \cdot V_{in})^2}{R_{load}}$$

If Vin doubles, to keep the equation valid, the power shall quadruple!







The DAB kernel Plot 1: The power curves





Click me!

The DAB kernel Plot 1: The power curves. What else does this imply?

• According to the plot 1 we set D1 > D2 (Always!).



The DAB kernel Plot 2: RMS values

- Locking the gain, the more Angle 1 or Angle 2 increases, the more the RMS values increases.
- Locking Angle 1 or Angle 2, the more the gain increases, the more the RMS values ... increase or decrease?



The DAB kernel Plot 3: ZVS @ turn on

• Gain = 1 enables a greater ZVS area respect the other gain conditions



Nover published

Real time <u>video</u>

The DAB kernel Subcases

Question for you: Which one is better?

• D1 > D2 : subcases



D1+D2 > 1 (or >180°) Example: Angle 1 = 180°, Angle 2 = 90°



The Role of the Leakage Inductance "LLK"



The DAB is an evolution of the PSFB

PSFB features

- Lower Leakage inductance to induce ZVS during the dead time
- high current on the secondary $\rightarrow E = 0.5 \cdot L \cdot I^2 \rightarrow$ Large output inductor to control the power (like the classical Buck/Forward converter)
- All secondary Fets work synchronously only in respect to the primary → no secondary phase control





	ANGLE 1	ANGLE 2	Pmax	lsw1 rms	ZVS
CASE 1	180	90	960	5,5	ALL
CASE 2	90	90	480	4	Not assured



	ANGLE 1	ANGLE 2	Pmax	lsw1 rms	ZVS
CASE 1	180	90	960	5,5	ALL
CASE 2	90	90	480	4	Yes Q3,Q4,Q5,Q6 Quasi Q1,Q2,Q7,Q8



	ANGLE 1	ANGLE 2	Pmax	lsw1 rms	ZVS
CASE 1	180	90	960	5,5	ALL
CASE 2	90	90	480	4	Yes Q3,Q4,Q5,Q6 Quasi Q1,Q2,Q7,Q8



	ANGLE 1	ANGLE 2	Pmax	lsw1 rms	ZVS
CASE 1	180	90	960	5,5	ALL
CASE 2	90	90	480	4	Yes Q3,Q4,Q5,Q6 Quasi Q1,Q2,Q7,Q8

CASE 1









From Plot 1

• Select the Angle 1 to avoid flat zones once Angle 2 is called to increase.

Potential choices are Angle 1 = 90° or Angle 1 = 180°

Notes:

- If Angle 2 = 90° and Angle 1 = 180° we can deliver the maximum possible power from this kernel (see <u>green</u> curves)
- Also the more the power requirement P_{eff} is, the less the leakage inductance value is, the more the size is. In fact: $L_{lk \ eff} \propto \frac{1}{k_p} \rightarrow$
 - but $k_p = \frac{P_{eff}}{P_{kernel}}$
- Both bunch of curves at Angle 1 = 90° and Angle1=180° give a good power shape while offering a different leakage inductance once the baseline kernel power is set. Angle1=180° could win because it is able to deliver more power while Angle 1= 90° could win because it is able to offer lower RMS current as we will see.

Takeaway

From Plot 1 • Angle 1 = 90° or Angle 1 =180°





From Plot 2

- Locking Angle 1, if Angle 2 increases then RMS current increases
- Locking Angle 2, if Angle 1 increases then RMS current increases (working point assumed to be on the right side of the gain threshold)

Potential choice is Angle 1 = 90 (low RMS)

From Plot 1 • Angle 1 = 90° or

Takeaway

Angle 1 =180°

From Plot 2 • Angle 1 = 90°



60 80 100 120 140 160

Plot 3: Full ZVS @ turn on

150

ନ୍ଥି ଅଧି-

P 130

120

110

100

20 40 60 80 100 120 140 160

............

•••••••••

00000000

~~9000

K: 90 Y: 95 000

....

Angle2 [deg]

Gain = 1.5
 Gain = 1
 Gain = 1.5

Angle2 [deg]

From Plot 3

- Select the best gain compromise between ZVS and deliverable power.
- If the gain < 1 we decrease ZVS area and we are able to deliver low power.
- If the gain > 1 we decrease ZVS area but we are able to deliver high power.
- If the gain = 1, by keeping Angle2 lower enough we guarantee the lower RMS current value possible, while keeping a discrete value of power delivery

Best compromise is Gain = 1 so Vor = Vin!

Notes:

- If Angle 2 = 90° with Angle 1 = 180° we get full ZVS
- If Angle 2 = 90° with Angle 1 = 90° we get quasi ZVS for some FETs

Best compromise is Angle 1 = 180 (full ZVS)

Takeaway

From Plot 1
Angle 1 = 90° or Angle 1 =180°

From Plot 2

• Angle 1 = 90°

From Plot 3

- Angle 1 = 180°
- Gain = 1







Trade off needed: Keep the Angle 1 = 180° (best ZVS condition) while keeping Angle 2 equal to the angle for which you get the same power by getting Angle1 = Angle2 = 90° (best RMS condition). Gain=1

All the designs will be scaled according to the kernel power equal to P = 480W



Trade off needed: Keep the Angle 1 = 180° (best ZVS condition) while keeping Angle 2 equal to the angle for which you get the same power by getting Angle1 = Angle2 = 90° (best RMS condition). Gain=1

All the designs will be scaled according to the kernel power equal to P = 480W

Sizing the Capacitors

Sizing Cout



Sizing C_dc_block (or move for current mode directly)

$$Z_{Llk} \gg Z_{C \ dc \ block}$$

$$2 \cdot \pi \cdot f \cdot L_{lk} \gg \frac{1}{2 \cdot \pi \cdot f \cdot C \ dc \ block}$$

$$C_{dc \ block} \approx 100 \cdot \frac{1}{4 \cdot \pi^2 \cdot f^2 \cdot L_{lk}}$$

Note:

avoid ripple criteria , we don't need to filter the noise – like Cout

Testing the DAB kernel - <u>Reversing the Power flow</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH



Testing the DAB kernel – <u>Load Regulation</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH

Angle2 [deg]



Load step

480W → 240W

Testing the DAB kernel – <u>Load Regulation</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH

Load step

480W → 240W





Testing the DAB kernel – Load RegulationLoad stepVin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52 μ HLoad step480W \rightarrow 240W

Angle 2 Imag peak CASE Angle 1 Vout Isw RMS Pout **Baseline 48** 26 0.1 A 180 480 W 1.9 A Pmax **Step Load** Α **48** 26 $180 \rightarrow 90$ 240 W **50mA** 1.34 A Pmax/2**Step Load** B 48 180 $26 \rightarrow 12$ 240 W 0.1 A 0.88 A Pmax/2


Testing the DAB kernel – Load Regulation Load step Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH 480W → 240W CASE A Circuit Changes: CASE B Circuit Changes: CASE A CASE B Rload \rightarrow 2 x Rload Rload \rightarrow 2 x Rload Angle 1: $180^\circ \rightarrow 90^\circ$ Angle 2: $26^\circ \rightarrow 12^\circ$ Angle 2: locked to 26° Angle 1: locked to 180° Vout Vout 50 50 40 40 30 Both are 30 20 20 Preferred valid, but I'll 10 10 go for the 0 0 -10 -10 right one Pout Pout 250 250 200 200 150 150 100 100 50 50 0 0 5m 10m 15m 20m 25m 30m 25m 30m 10m 20m 0 5m 15m

Time (s)

37

Time (s)

Testing the DAB kernel – <u>Bus Regulation</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH



The Gain is <u>NOT</u> constant (0.5 here) while the Power shall be constant!

Bus step

 $200V \rightarrow 400V$

3rd scaling law: '...Vin x2 gives Pout x 4...' so Pout ÷ 4 on the power curves gives 480:4=120W @ gain = 0.5

SOLUTIONS

	Angle 1	Angle 2	
CASE A	Locked to 180°	26.5° → 12°	
CASE B	180° → 90°	Locked to 26.5°	
CASE n	Whatever combo gives 120W		

Testing the DAB kernel – <u>Bus Regulation</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH



The Gain is <u>NOT</u> constant (0.5 here) while the Power shall be constant!

Bus step

 $200V \rightarrow 400V$

3rd scaling law: '...Vin x2 gives Pout x 4...' so Pout ÷ 4 on the power curves gives 480:4=120W @ gain = 0.5

SOLUTIONS

	Angle 1	Angle 2	
CASE A	Locked to 180°	26.5° → 12°	
CASE B	180° → 90°	Locked to 26.5°	
CASE n	Whatever combo gives 120W		

Solution B is better by the RMS side

Testing the DAB kernel – <u>Bus Regulation</u> Bus step Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH $200V \rightarrow 400V$



The Gain is <u>NOT</u> constant (0.5 here) while the Power shall be

'....Vin x2 gives Pout x 4....' so Pout ÷ 4 on the power curves gives 480:4=120W @ gain = 0.5

	Angle 1	Angle 2	
CASE A	Locked to 180°	26.5° → 12°	
CASE B	180° → 90°	Locked to 26.5°	
CASE n	Whatever combo gives 120W		

Both Solutions do not guarantee full ZVS (we are out of the <u>green</u> area @ gain=0.5)

Testing the DAB kernel – <u>Bus Regulation</u> Bus step Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH $200V \rightarrow 400V$ CASE A Circuit Changes: CASE B Circuit Changes: CASE A CASE B $Vin \rightarrow 2 \times Vin$ Vin \rightarrow 2 x Vin Angle 1: locked to 180° Angle 2: locked to 26° Angle 1: 180° → 90° Angle 2: $26^\circ \rightarrow 12^\circ$ Vout Vout 50 50 40 40 Both are 30 30 20 20 valid, but I'll referred 10 10 go for the 0 -10 -10 right one Pout Pout 500 500 400 400 300 300 200 200 100 100 0

5m

0

10m

20m

15m

Time (s)

25m

30m

25m

20m

30m

5m

0

10m

15m Time (s)

Testing the DAB kernel – <u>Variable Vout</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH



The Gain is <u>NOT</u> constant (1.5 here) while the Power shall be constant!

Constant

480W over

 $48V \rightarrow 72V$

If we need « flat power » at 72V@480W then Rload <u>cannot</u> be the same as 48V@480W ! 3rd scaling law: Vout x1.5 gives Pout x 2,25! Or equivalently Vout x1.5 gives Rload x 2,25

SOLUTIONS

	Angle 1	Angle 2	
CASE A	Locked to 180°	26.5° → 16.5°	
CASE B	180° → 90°	26.5° → 38°	
CASE n	Whatever combo gives 480W		

Testing the DAB kernel – <u>Variable Vout</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH



The Gain is <u>NOT</u> constant (1.5 here) while the Power shall be constant!

Constant

480W over

 $48V \rightarrow 72V$

If we need « flat power » at 72V@480W then Rload <u>cannot</u> be the same as 48V@480W ! 3rd scaling law: Vout x1.5 gives Pout x 2,25! Or equivalently Vout x1.5 gives Rload x 2,25

SOLUTIONS

	Angle 1	Angle 2	
CASE A	Locked to 180°	26.5° → 16.5°	
CASE B	180° → 90°	26.5° → 38°	
CASE n	Whatever combo gives 480W		

Solution A is better by the RMS side



The Gain is <u>NOT</u> constant (1.5 here) while the Power shall be constant!

If we need « flat power » at 72V@480W then Rload <u>cannot</u> be the same as 48V@480W ! 3rd scaling law: Vout x1.5 gives Pout x 2,25! Or equivalently Vout x1.5 gives Rload x 2,25

SOLUTIONS

	Angle 1	Angle 2	
CASE A	Locked to 180°	26.5° → 16.5°	
CASE B	180° → 90°	26.5° → 38°	
CASE n	Whatever combo gives 480W		

Both Solutions do not guarantee full ZVS (we are out of the <u>blue</u> area @ gain=1.5)

Testing the DAB kernel – <u>Variable Vout</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52 μ H Constant 480W over 48V \rightarrow 72V



Testing the DAB kernel Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH

SUMMARY					
System Perturbation	Preferred Solution	Reasons			
Load Step	Control Angle 2	One control variable and lower RMS ZVS preserved			
Bus step	Control Angle 1	Same as above ZVS not assured			
Flat Power over Vout variations	Control Angle 2	Same as above ZVS not assured			

Testing the DAB kernel Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH



"Could we target Angle2 >26°, trying to preserve ZVS vs huge bus Step?" Absolutely yes. It's strongly dependent from the requirements!



DAB Design 1 Pout = 7 kW, Vout = 48V, Vin = 380V, fsw = 100kHz

Assumptions

48

- Best entry Angles are Angle 1 = 180° and Angle $2 \approx 26^{\circ}$
- Best gain entry point is: gain = 1

Before: calculate the scaling factors!





After: calculate the Leakage inductance, the turn ratio and both capacitors):

$$L_{Lk} = \frac{L_{kernel}}{k_f \cdot k_p} = \frac{52 \ uH}{4} = 12,8 \ uH \qquad \qquad C_{dc \ block} \approx 100 \cdot \frac{1}{4 \cdot \pi^2 \cdot f^2 \cdot L_{lk}} \approx 20\mu$$

$$N = \frac{N_p}{N_s} = \frac{380}{48} = 7.91 \qquad \qquad C_{out} \approx \left(I_{Llk \ peak} \cdot \frac{N_p}{N_s} - \frac{P_{out}}{V_{out}}\right) \cdot \frac{\frac{T}{2} - T_{angle2}}{\Delta V_{out \ (1V)}} \approx 110\mu$$

DAB Design 1 Pout = 7 kW, Vout = 48V, Vin = 380V, fsw = 100kHz



Questions



- What if we have D2 > D1?
- What if we run the DAB in synchronous mode?
- What if the gain varies?



Inductor equation (valid for all cases):

$$V_L = L \cdot \frac{\Delta I}{\Delta t} \to \Delta I = \frac{V_L}{L} \cdot \Delta t \to \Delta I = \left[\frac{\left(V_p + V_{or}\right)}{L} \cdot T_{D2} + \frac{\left(V_p - V_{or}\right)}{L} \cdot \left(\frac{T_s}{2} - T_{D2}\right)\right]$$

Angle 1 = 180° Angle 2 = 26° ;

gain = 1,5 (\uparrow Power , \downarrow ZVS, \uparrow RMS)



Question for you: Are you able to catch instantly which FET over 8 enables ZVS?

DAB Design 2 Pout = 200 kW, Vout = 800V, Vin = 300V, fsw = 85kHz

Assumptions

- Best entry Angles are Angle 1 = 180° and Angle $2 \approx 26^{\circ}$
- Best gain entry point is: gain = 1

Before: calculate the scaling factors!





After: calculate the Leakage inductance, the turn ratio and both capacitors):

$$L_{Lk} = \frac{L_{kernel}}{k_f \cdot k_p} = 331n$$

$$N = \frac{N_p}{N_s} = 0,375$$

$$C_{dc \ block} \approx 100 \cdot \frac{1}{4 \cdot \pi^{2} \cdot f^{2} \cdot L_{lk}} \approx 1m$$

$$C_{out} \approx \left(I_{Llk \ peak} \cdot \frac{N_{p}}{N_{s}} - \frac{P_{out}}{V_{out}} \right) \cdot \frac{\frac{T}{2} - T_{angle2}}{\Delta V_{out \ (1V)}} \approx 185 \mu F$$

DAB Design 2 Pout = 200 kW, Vout = 800V, Vin = 300V, fsw = 85kHz



LLC Design comparison Pout = 200 kW, Vout = 800V, Vin = 300V, fres HI = 110kHz

	LLC	DAB
Vbus [V]	300	300
fsw [kHz]	85	85
LIK [H]	250n	331n
Lmag [H]	2,25µ	100µ
C dc Block [F]	-	1m (optional)
C res [F]	8.34 µ	-
lsw1 RMS [A]	585	530
Lm/L_Lk	9	-
Angle 1 Angle 2	-	180 26
Turns Ratio	0.393	0.375



- Vout is perfectly superimposed in steady state
- DAB is slower due to higher electrical values (higher time constants)



Deep ZVS @ turn on for DAB and LLC



- With Angle 1 = 180, Angle 2 = 26, RMS current is lower for the DAB.
- LLC Lratio = Lm/Llk = 9 (high inductance ratio used for the LLC to keep low RMS).
- LLC assures ZCS on both : On and Off on the secondary, the DAB doesn't with PS modulation.



With Angle 1 = 180, Angle 2 = 26, Iprimary peak is lower for the DAB, as well as the RMS

LLC Design comparison Pout = 200 kW, Vout = 800V, Vin = 300V, fres HI = 110kHz

	DAB							
Conduction	l Losses		Switch	ning	g Lo:	sses OFF		
Irms1[A]	530		Imax1	[A]	750)		
Irms5 [A]	130		Imax5	[A]	300)		
Rds on [Ohm]	0.01		tcross	[s]	1.5	0E-08		
Q1 [W]	2809		Q1 [W]		143	3.44		2952.438
Q5 [W]	169		Q5 [W]		153	6		322
x4 Mos Pri								11809.75
x4 Mos Sec								1288
Efficiency	0.938536	5						13097.75
	/			_				
				.C			1	
Conduction	Losses		S	wit	chir	ig Losses		Ploss tot
Irms1[A]	580		Im	ax1	[A]	350		
lavg5 [A]	125		Im	ax5	[A]	NA		
Rds on [Ohm]	0.01		tcr	oss	[s]	1.50E-08		
Q1 [W]	3364		Q1	[W]	6.69E+01		3430.938
Q5 [W]	62.5		Q5	[W]	NA		62.5
x4 Mos Pri		Ļ						13723.75
x4 Mos Sec								250
Efficiency	0.934694							13973.75



Coincidence! What we gain in RMS with DAB is gained with free ZCS in LLC. Electrical Performance is quite similar here, but a crosscheck comparison is always recommended for the specific application. What about magnetics volume and their losses?



 $B_{peak} = \frac{L}{N \cdot A_e} \cdot I_{peak} \rightarrow \begin{cases} L \cdot I_{peak \, DAB} \approx 1000 \mu \\ L \cdot I_{peak \, LLC} \approx 800 \mu \end{cases}$

LLC Design comparison Pout = 200 kW, Vout = 800V, Vin = 300V, fres HI = 110kHz

Fast prototyping from Sunlord Magnetics

	DAB	LLC	
Core (custom)			
Dimensions [cm]	13.4 x 10.4 x 9	same	
L_pri [µH]	100	2.25	
L_sec [µH]	600	14	
L_Lk [µH]	0.33	0.25	
Turns ratio [pri/sec]	$2:5 \pm 0.5$	same	
DCR pri [mΩ]	0.5	same	
DCR sec $[m\Omega]$	2	same	
Layers	6 pri / 5 sec	same	
GAP [mm]	No gap	14	
Losses [W]		≈ 250	

Sunlord

Focal point: Max Soriano max_soriano@sunlordinc.com

Detailed datasheet available

55

LLC vs DAB Takeaway

	LLC	DAB	Notes
Soft Switching	Yes with limitations	Yes with limitations	LLC: If the working point falls in the «middle frequency range» between resonances then Soft switching is assured on both sides primary ZVS and secondary ZCS. DAB: To assure ZVS soft switching there are two degrees of freedom: Modulation Angles and gain. Or move for advanced modulation techniques (es: triangular, trapezoidal modulations etc.)
Isolation	YES	YES	
RMS current	585 (Pout=200k)	530 (Pout=200k)	LLC RMS currents are Lratio=Lm/Llk dependent, so keep it high being careful to the frequency variation range over the Vbus swing. If Lratio ↑, then RMS ↓, while fspan ↑ vs Vbus step. DAB RMS currents are modulation angles and gain dependent. If their selection will be Angle1 = 180 and Angle 2=26 then Soft switching is assured on both sides, plus lower RMS current will be guaranteed.
Frequency	Variable	Fixed	
Components	Higher	Lower	DAB: does not require C_dc_Block if used with Current Mode Contol LLC: does require a secondary side cap. if used in reverse power flow otherwise Vout clamps Lmag. Also, resonant Cap on the primary is required to get resonant action
Bidirectionality	Possible	Possible	
Scalability	Hard	Medium	Easy to replace magnetics; Hard to replace Caps for the LLC due to Layout limitations. Investigate current sharing capability: Hard with variable frequency, but feasible.
Control	Medium	Hard	DAB: requires 8 switches to be controlled. Passive (or synch.) secondary not recommendend because the power falls dramatically. In this case it's convenient to reivent the PSFB adding, Lout. LLC: requires just 4 switches to be controlled with primary Full Bridge; or 2 switches only in Half Bridge mode. Passive secondary assumed for the LLC.
Efficiency	High	High	
Primary Bridge	Half / Full	Full	Volume and cost impact
Secondary Bridge	Half / Full	Full	Volume and cost impact

Ending notes

 \succ Check always Soft Switching \rightarrow look at the waveforms

No particular math needed: Ohm's law only. "It's easy to be dazzled by the apparent power of mathematics but please resist the temptation to take refuge in complex equations to understand how the circuit really works". [Horowitz – Hill. The Art of Electronics - Chap 4]

- Sweeping Angles gives much more info than mathematical formulas !
- > Combine N. Rosano's plots with S. Maniktala Scaling Laws

Question for you: Did you notice, for the DAB, we didn't talk about Lmag? Why didn't we call out a specific value for Lmag in all examples?



Advanced DAB Topics

Advanced modulation techniques Full Soft Switching : ZCS and ZVS





How can we get these?

- Select a suitable topology which automatically enables soft switching
- Acting on the control «forcing» soft switching
- Advanced modulation techniques: triangular, trapezoidal, combined etc.

What do we need to look at in the DAB?

- Voltages (Vp and Vor)
- Currents (leakage current)

Advanced modulation techniques Full Soft Switching : ZCS and ZVS





How can we get these?

- Select a suitable topology which automatically enables soft switching
- Acting on the control «forcing» soft switching
- Advanced modulation • techniques: triangular, trapezoidal, combined etc.

What do we need to look at in the DAB?

- Voltages (Vp and Vor)
- Currents (leakage current)

Switch here to get ZCS but we cannot assure fixed phase shift

RLOAD · N²

COUT/N²

Testing the DAB kernel – <u>Deadtime effects</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH



Testing the DAB kernel – <u>Deadtime effects</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH



Solution:

Keep the dead time not so short to enable Cds discharge, as well as not so long increasing antiparallel diode losses plus the output power drop effect. Td is strongly dependent on the application (leakage inductance – Fet selection VS working conditions).

Testing the DAB kernel – <u>Deadtime effects</u> Vin=200V; Vout=48V; P=480W; fsw=100k; gain=1; LLk=52µH



Hardware



Solution:

Keep the dead time not so short to enable Cds discharge, as well as not so long increasing antiparallel diode losses plus the output power drop effect. Td is strongly dependent on the application (leakage inductance – Fet selection VS working conditions).

Understanding the transformer action



Nicola Rosano Projects









(12) United States Patent Maniktala et al.

(10) Patent No.: US 10,804,726 B2
(45) Date of Patent: Oct. 13, 2020





 SW / 6.78MHz
 SW / > 100 kHz

 Image: SW / 6.78MHz
 SW / > 100 kHz

 Image: SW / 6.78MHz
 Image: SW / < 100 kHz</td>

 Image: SW / 6.78MHz
 Image: SW / < 100 kHz</td>

 Image: SW / 6.78MHz
 Image: SW / < 100 kHz</td>

 Image: SW / 6.78MHz
 Image: SW / < 100 kHz</td>

 Image: SW / 6.78MHz
 Image: SW / < 100 kHz</td>

 Image: SW / 6.78MHz
 Image: SW / < 100 kHz</td>

 Image: SW / 6.78MHz
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: SW / < 100 kHz</td>
 Image: SW / < 100 kHz</td>

 Image: S

Look at power vs dimensions (Chargedge RX)





ChargeEdge is open to collaborations!

Nicola Rosano: nicolarosano85@gmail.com

Contacts: Gregory Clark: <u>gregg@chargedge.com</u> Robert Tetrault: <u>bob.tetrode@gmail.com</u>



Acknowledgements

- Ray Ridley, for hosting me and his massive contribution to our world as well as his
 patience to give technical support to all power electronics engineers.
- Power Supply Design <u>FaceBook Goup</u>
- Ridley Engineering <u>Power Supply Design Center</u>


Power Supply Design Center

Private group · 5.9K members



Hands-On Workshop **Magnetics**, Topologies **And Control**

[114] TRANSIENT LOOP SWEEPS OUTPERFORM SMALL-SIGNAL MODELS

FEATURED ARTICLE: [111] ZVS FULL-BRIDGE CONVERTER EMPLOYING AN ACTIVE SNUBBER

10 uniday

[102] CUSTOM INDUCTORS - ONE DESIGN EQUATION



[A21] DESIGNING WITH THE TL431





[083] NONINVASIVE LOOP GAINS [A08] SIX COMMON REASONS FOR FROM OUTPUT IMPEDANCE POWER SUPPLY INSTABILITY MEASUREMENTS





6 6 6 Innter 6 6



Design Software Version 15 with LLC

Our Most Popular Webinars

Our Most Popular Design Center Articles



Definitive Free Book on **Current-Mode**



